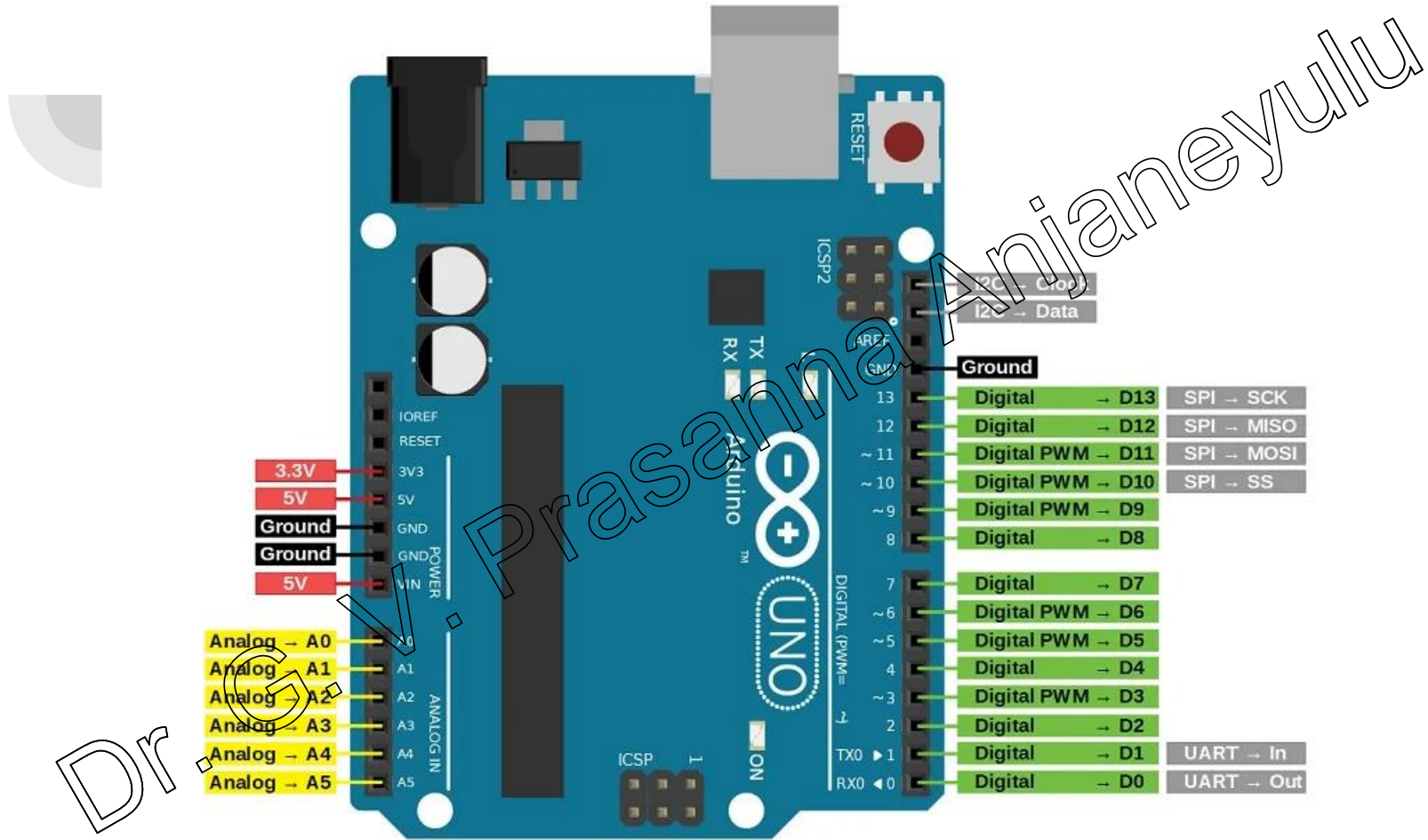


8.DC_Motor Speed & Direction Control

With ARDUINO

Dr. G. V. Prasanna

Anjaneyulu



Note



In built microcontroller can't run DC motor because motor draws large current


Even if it runs, but it cannot reverse the direction of motor

So L293D driver IC is used

With this IC 2-DC motors are controlled at a time


Dr. G. V. Prasanna Anjaneyulu

L293D Driver-IC

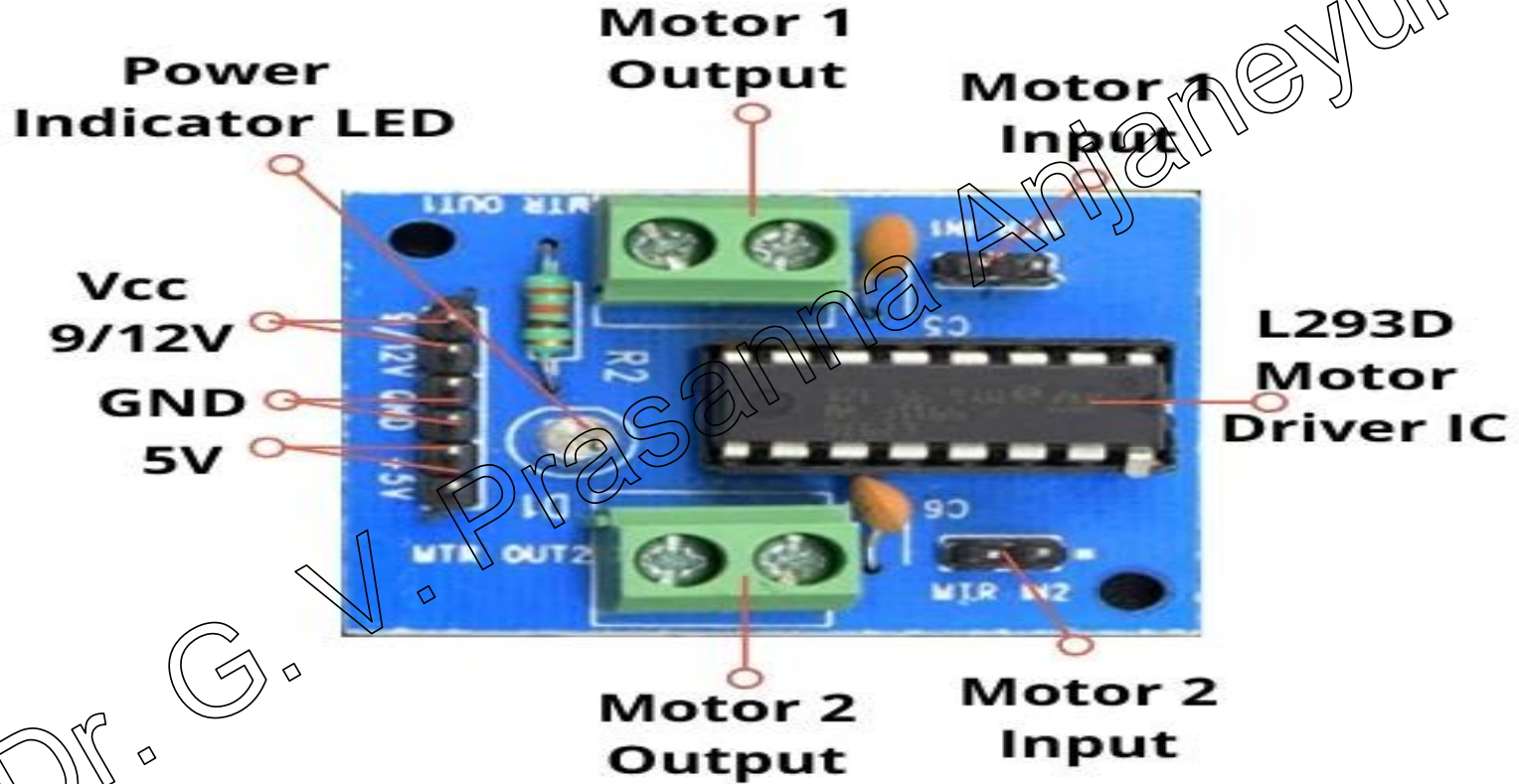

Apparatus

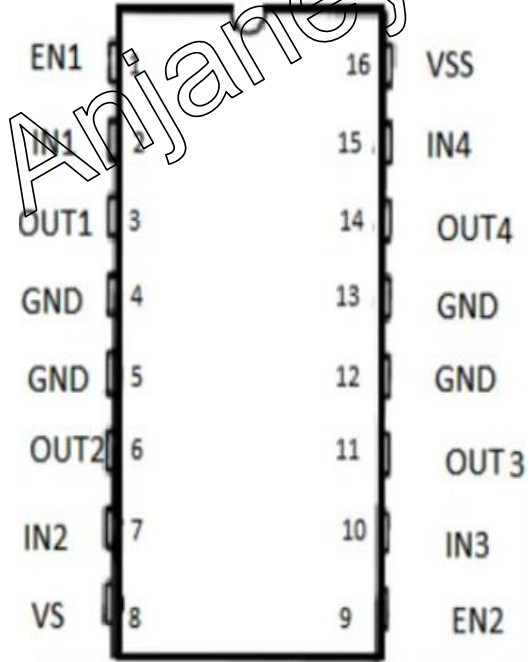- 1.PC with Arduino IDE
- 2.Arduino UNO Board
- 3.USB cable
- 4.DC motor
- 5.Bread board
- 6.1k Ω resistor
- 7.Jumper wires
- 8.L293D motor IC




L293D Motor Driver IC

By using this we can control 2-motors at a time, but here using for 1-motor control only.


For Speed control EN1, EN2 used


For Direction control IN1-IN2, IN3-IN4 used

Speed Control

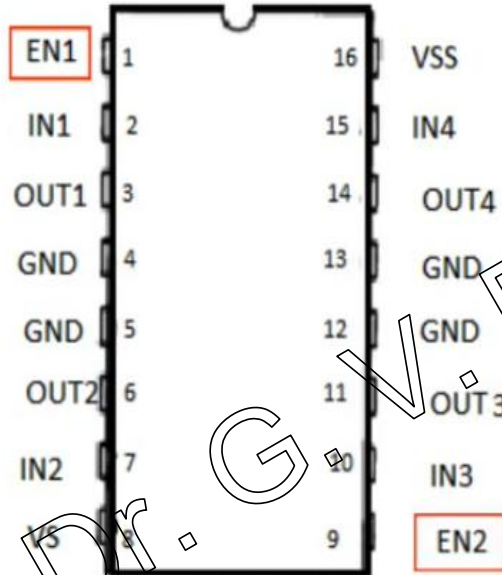

Direction Control

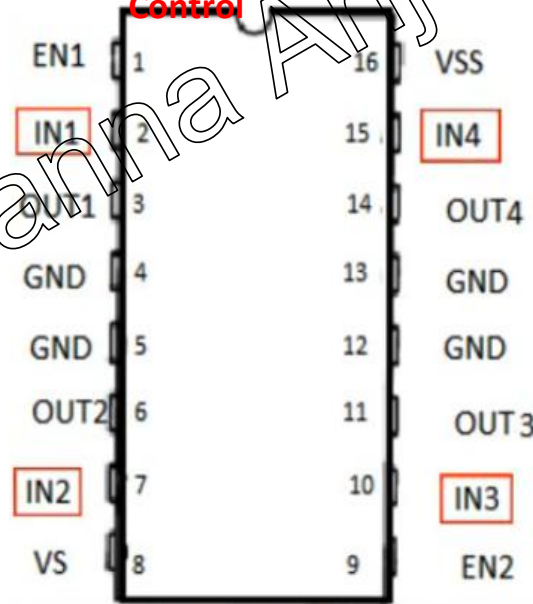

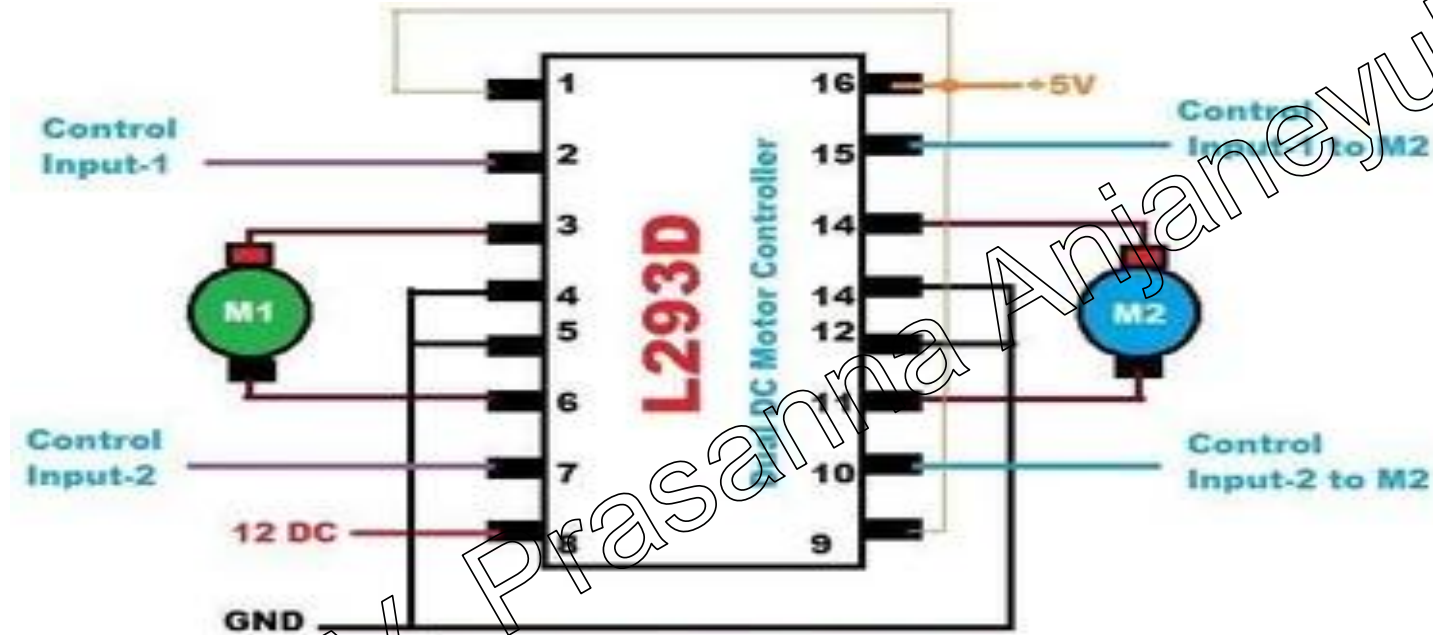

Dual H-Bridge Circuit using L293D


All inputs Low: Motor M1 & M2 = OFF.

Input-1 is High and Input-2 is Low: Motor M1 = Forward Direction.

Input-1 is Low and Input-2 is High: Motor M1 = Backward Direction.

Same Condition to M2.

Single DC motor Control circuit

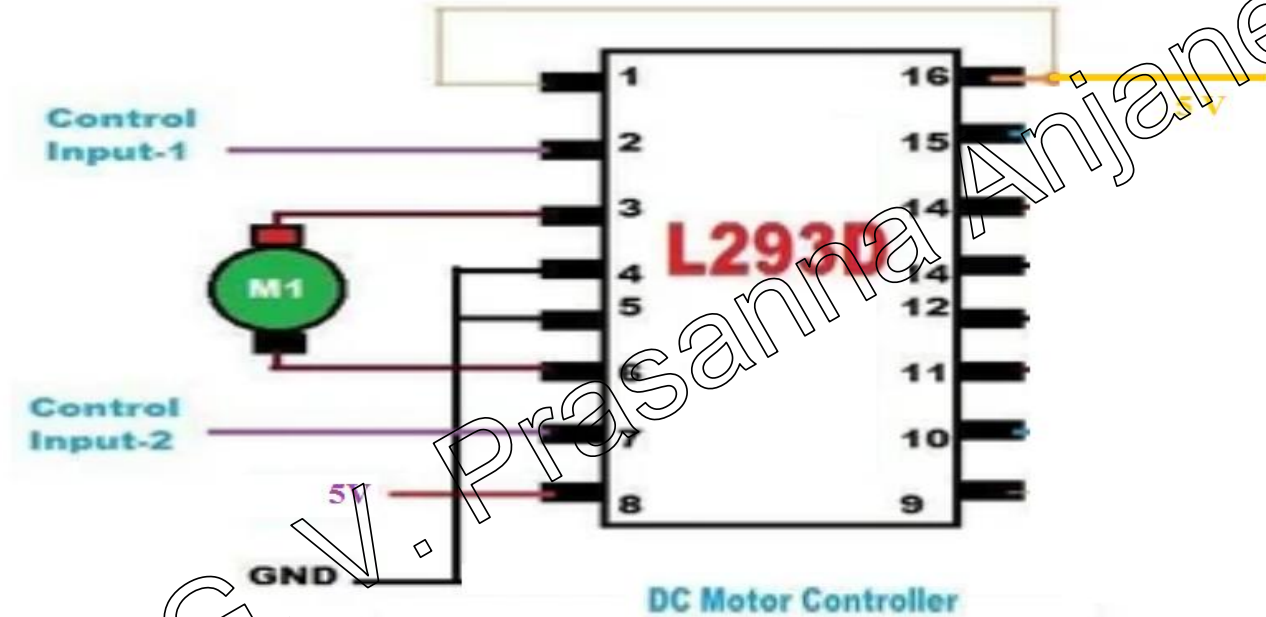


All inputs Low: Motor M1 = OFF.

Input-1 is High and Input-2 is Low: Motor M1 = Forward Direction.

Input-1 is Low and Input-2 is High: Motor M1 = Backward Direction.

Circuit Diagram

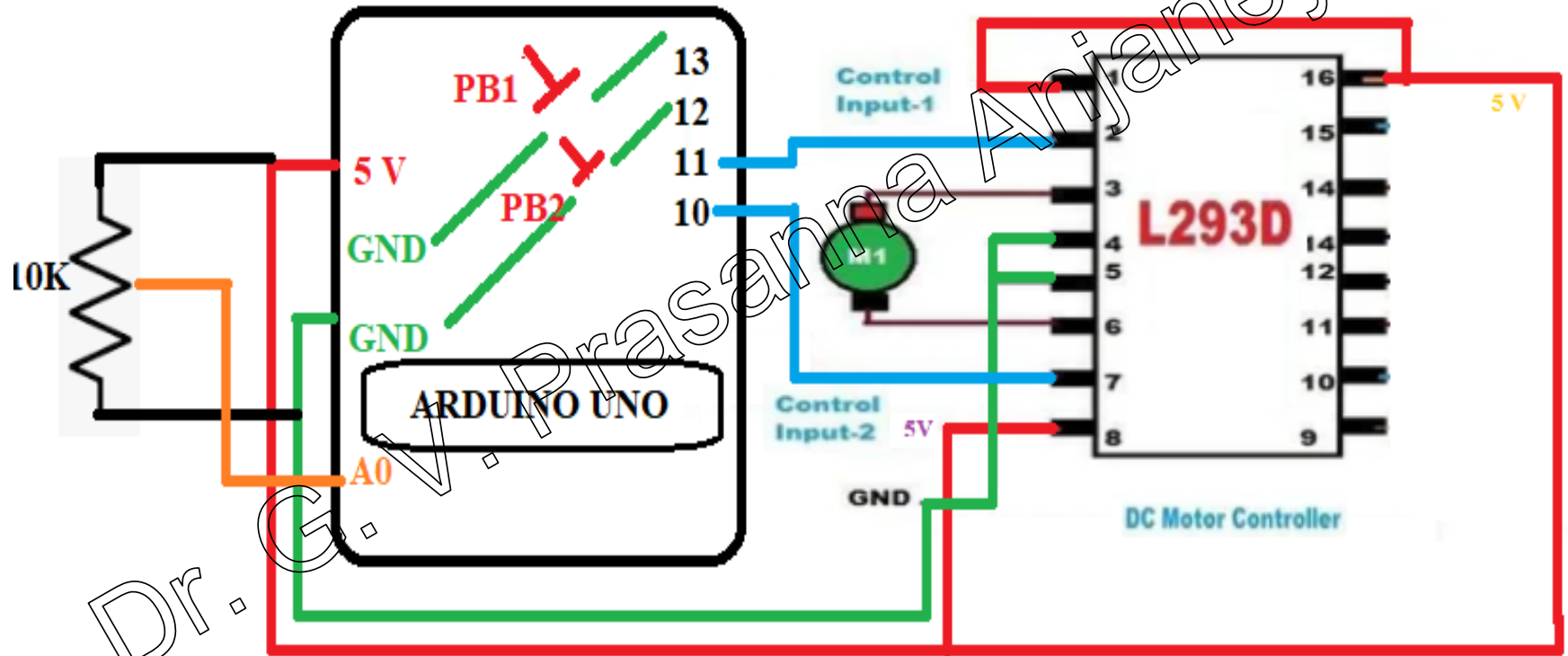

Program

```
// speed_direction_control_DC-Motor
const int potPin = A0;
const int fwdbuttonPin = 13;
const int bckbuttonPin = 12;
const int ICpin2 = 11;
const int ICpin7 = 10;
int potValue = 0;
int motorValue = 0;
int fwdbuttonState = 0;
int bckbuttonState = 0;

void setup()
{
  pinMode(fwdbuttonPin, INPUT_PULLUP);
  pinMode(bckbuttonPin, INPUT_PULLUP);
  pinMode(ICpin2, OUTPUT);
  pinMode(ICpin7, OUTPUT);
}
```

```
void loop()
{
  potValue = analogRead(potPin);
  motorValue = map(potValue, 0, 1023, 0, 255);
  fwdbuttonState = digitalRead(fwdbuttonPin);
  bckbuttonState = digitalRead(bckbuttonPin);
  delay (500);
  if(fwdbuttonState == LOW || bckbuttonState == LOW)
  {
    analogWrite(fwdbuttonState == LOW ? ICpin2 : ICpin7, motorValue);
    digitalWrite(fwdbuttonState == LOW ? ICpin7 : ICpin2, LOW);
  }
  else
  {
    digitalWrite(ICpin2, LOW);
    digitalWrite(ICpin7, LOW);
  }
}
```

Circuit Diagram

